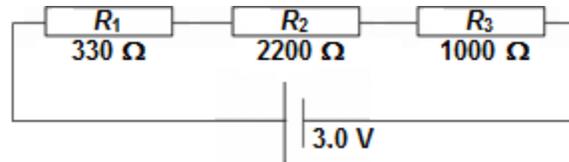


Show formulas, substitutions, answers (in spaces provided) and units!

A series circuit powered by a 3.0 V cell is shown.




15. What is the total or equivalent resistance of this circuit?
15. _____

16. What is the current through this circuit?
16. _____

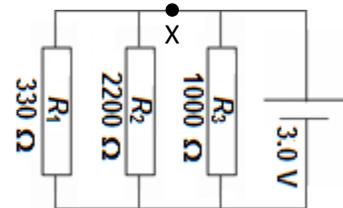17. What are the voltages across each resistor?
17. $V_1 =$ _____
 $V_2 =$ _____
 $V_3 =$ _____

A parallel circuit powered by a 3.0 V cell is shown.




18. What is the total or equivalent resistance of this circuit?
18. _____

19. What is the current through the cell?
19. _____

20. What are the currents through each resistor?
20. $I_1 =$ _____
 $I_2 =$ _____
 $I_3 =$ _____

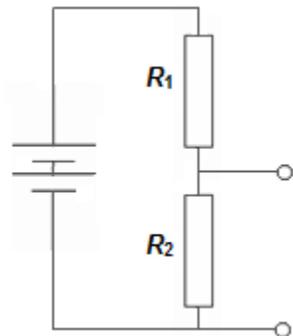21. What is the current through the point X?
21. _____

A series circuit powered by a battery whose voltage is 6.0 V is shown in the schematic diagram.




22. Label V_{OUT} and V_{IN} in this circuit.
22. In diagram

23. Suppose the value of R_1 is 2400 Ω . If we would like to “create” 1.5 V at V_{OUT} what should the value of R_2 be?
23. _____

24. Suppose the value of R_2 is 2400 Ω . If we would like to “tap” 1.5 V at V_{OUT} what should the value of R_1 be?
24. _____

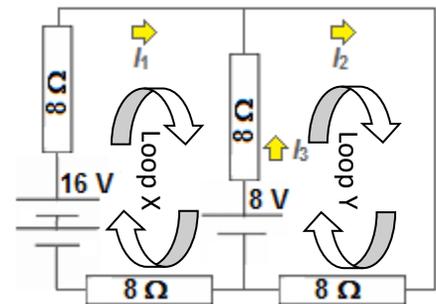25. What is this type of circuit called?
25. _____

A circuit constructed of resistors and two voltage sources is shown.



26. Use Kirchhoff’s rule for I and write the current equations for each junction.
26. _____

27. Use Kirchhoff’s rule for V and write the voltage equation for Loop X.
27. _____

28. Use Kirchhoff’s rule for V and write the voltage equation for Loop Y.
28. _____

29. Find the values of the three currents and the four resistor voltages. Write them in the diagram.